

Current Electricity

- Cells consist of different types of metals in an acidic or basic bath that provide a potential difference called an electromotive force (EMF) (Voltage / Potential difference)

EMF \therefore cell provides a potential that causes charges to flow around a circuit.

- In a conductor, the # of number of charges passing a given point, in a unit of time is called current

$$I = Q/\Delta t$$

Unit of current: Coulombs / Second = Amps.

ex. 1 trillion electrons flow past a point in 0.50 s, what is current?


$$I = Q/\Delta t$$

$$I = 1 \times 10^{12} \times 1.6 \times 10^{-19} \div 0.50 =$$

- Conventional current: flows in the direction positive charges would move, even though electrons are moving the opposite.

- In old convention, we still use current flow from positive terminal to negative terminal. [but reality is the opposite]

Diagram Representation:

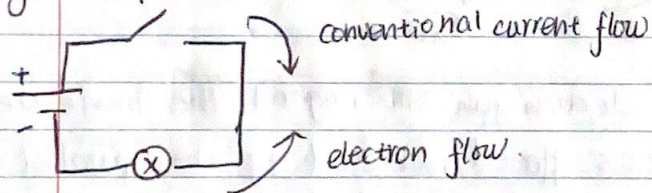

- Voltage is the reason that electrons to move

Problems: # 7, 25, 60.

- Electrical Power:

$$\text{Power} = \frac{E}{t} = \frac{Q \cdot V}{t} = IV \quad \therefore \boxed{P = IV} \quad \boxed{P = \frac{E}{t}} \quad (\text{units: Watts, J/s})$$

Electrical energy is in kW·h (kilowatt hour)


$$\text{Kilo Watt} \cdot \text{hour} = 1000 \text{ J/s} \times 3600 = 3.6 \times 10^6 \text{ J} \quad [\text{it costs } 14 \text{ cents in } 2018]$$

Example: How much does it cost to run a 1000 Watt hairdryer for 10.0 minutes.

Solution: $1000 \text{ Watts} \times \frac{1 \text{ kW}}{1000 \text{ W}} \times 10 \text{ minutes} \times \frac{1}{60 \text{ minutes}} \times \$0.14 \text{¢/kW}\cdot\text{h} = \$0.024.$

• Schematic Diagrams

Circuit Symbol:

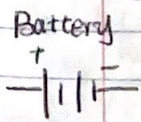

Wire



Junction



Resistor



Bulb





Switch



Voltmeter




Ammeter

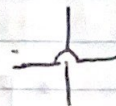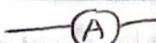


(No contact)

• Meter placement:

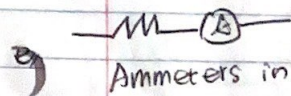

Ammeters in series.

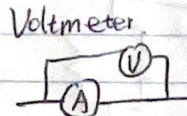

Voltmeter in parallel, across the device.

• An ideal magical ammeter would have 0 resistance.


• An ideal magical voltmeter would have infinite resistance (no current flow through)

Ohm's Law >>



Resistance in a circuit is like friction on a moving object, it impedes the flow of charge.

$$V = IR \quad (\text{Resistance} = \Omega \text{ Ohms})$$

Resistor symbol

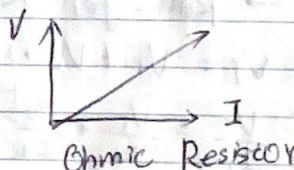

A conductor:

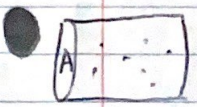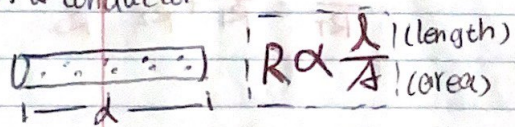

$$R = \frac{\rho l}{A}$$

[row]

(ρ : resistivity : $\Omega \cdot \text{m}$)

$\left\{ \begin{array}{l} l : \text{length (m)} \\ A : \text{area } \text{m}^2 \end{array} \right\}$

20.4.

Read 20.2 and 20.3, problems #12, 29.


Power Dissipated by a Resistor

$$\begin{aligned} V &= I \cdot R \\ P &= I V \end{aligned} \gg \therefore P = I^2 R \quad (\text{J/s})(\text{W})$$


$$\begin{aligned} P &= I V \\ I &= \frac{V}{R} \end{aligned} \gg \therefore P = \frac{V^2}{R} \quad (\text{J/s})(\text{W})$$

→ Circuit Analysis

• Series Circuit:

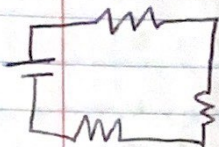

• Parallel Circuit

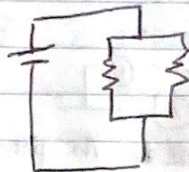

• In Parallel Circuits:

$$V_T = V_1 = V_2$$

$$I_T = I_1 + \dots + I_2$$

• In a Series Circuit:

$$V_T = V_1 + \dots + V_2$$

$$I_T = I_1 = I_2$$

→ Rules for R_T

• Series: $V_T = V_1 + V_2 + V_3$

$$\therefore \frac{V_T}{I_T} = \frac{V_1}{I_1} + \frac{V_2}{I_2} + \frac{V_3}{I_3}$$

(note: $I_T = I_1 = I_2 = I_3$)

$$\therefore R_T = R_1 + R_2 + R_3$$

(sum of Resistance)

• Parallel: $I_T = I_1 + I_2 + I_3$

$$\frac{I_T}{V_T} = \frac{I_1}{V_1} + \frac{I_2}{V_2} + \frac{I_3}{V_3}$$

(note: $V_T = V_1 = V_2 = V_3$)

$$\therefore \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

VIR chart

V	I	R
V_T 9.0	I_T 0.05	R_T 180 Ω
V_1 4.0	I_1 0.05	R_1 80 Ω
V_2 5.0	I_2 0.05	R_2 100 Ω

