

20.4.

Read 20.2 and 20.3, problems. #12, 29.

Power Dissipated by a Resistor

$$V = I \cdot R \quad \gg \quad \therefore P = I^2 R \quad (\text{J/s})(\text{W})$$


$$P = IV$$

$$P = IV \quad \gg \quad \therefore P = \frac{V^2}{R} \quad (\text{J/s})(\text{W})$$


$$I = \frac{V}{R}$$

→ Circuit Analysis

• Series Circuit:

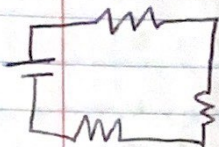

• Parallel Circuit

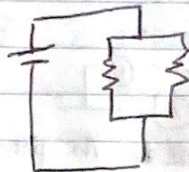

• In Parallel Circuits:

$$V_T = V_1 = V_2$$

$$I_T = I_1 + \dots + I_2$$

• In a Series Circuit:

$$V_T = V_1 + \dots + V_2$$

$$I_T = I_1 = I_2$$

→ Rules for R_T

• Series: $V_T = V_1 + V_2 + V_3$

$$\therefore \frac{V_T}{I_T} = \frac{V_1}{I_1} + \frac{V_2}{I_2} + \frac{V_3}{I_3}$$

(note: $I_T = I_1 = I_2 = I_3$)

$$\therefore R_T = R_1 + R_2 + R_3$$

(sum of Resistance)

• Parallel: $I_T = I_1 + I_2 + I_3$


$$\frac{I_T}{V_T} = \frac{I_1}{V_1} + \frac{I_2}{V_2} + \frac{I_3}{V_3}$$

(note: $V_T = V_1 = V_2 = V_3$)

$$\therefore \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

VIR chart

V	I	R
V_T 9.0	I_T 0.05	R_T 180 Ω
V_1 4.0	I_1 0.05	R_1 80 Ω
V_2 5.0	I_2 0.05	R_2 100 Ω

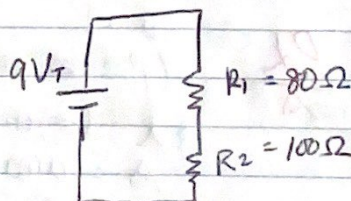


More Sophisticated Circuit Analysis.

Equivalent Resistance: R_{eq} or R_T .

The one resistor that can replace a network of resistors.

Ex ① $\begin{array}{c} \text{---} \text{---} \text{---} \\ R=10\Omega \quad R=20\Omega \quad R=15\Omega \end{array} = \text{---} \\ R=45\Omega$

② Parallel Circuit:



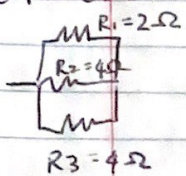


$R_T = 1\Omega$

$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

$R_T = \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{4}} = 1\Omega$




③ Net work:

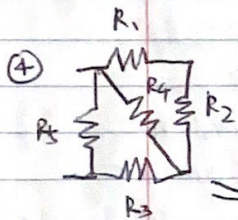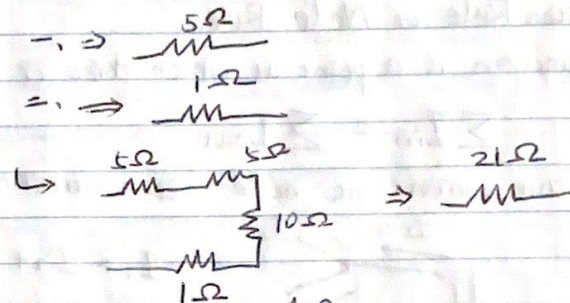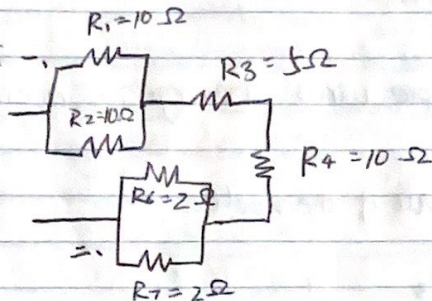

All R_s are 2Ω .


combine R_1 and $R_2 \Rightarrow 4\Omega$

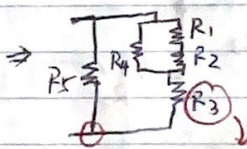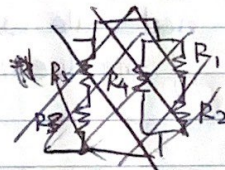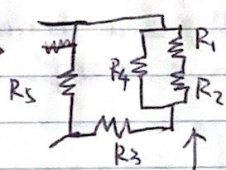combine R_3 and $R_4 \Rightarrow 4\Omega$ (X)



you can connect R_1, R_2 because they are directly connected, in series.

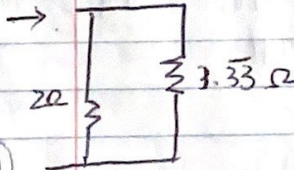
we can only put R_3 in parallel of R_5 because there is a third wire, not in series.



$\therefore R_T = \left(\frac{1}{2} + \frac{1}{3.33} \right)^{-1} = 1.25\Omega$

Reversed.

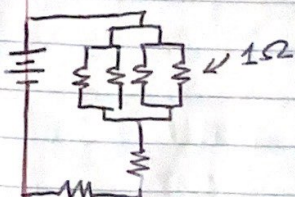Build a network of 4Ω resistors such that R_T or $R_{eq} = 9\Omega$.



Trick: To build one 1Ω resistance, we use the same # of the resistor's resistance, in parallel.
ex. 4 4Ω s in parallel.


Kirchoff's Laws

• Junction Rule or Node Rule:


A junction is a point at which three or more wires converge in a circuit.

$$\sum I_{in} = \sum I_{out}$$

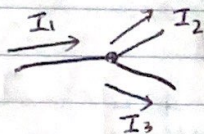sum current into node = sum current out of the node.




$$I_1 = I_2 + I_3$$

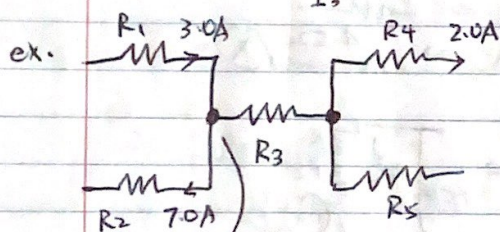

The direction is important, however, the node rule will give a negative answer if the direction is wrong.

Work:

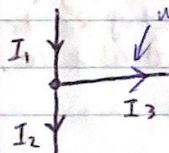

$$\sum I_{in} = \sum I_{out}$$

$$I_1 = I_2 + I_3$$

$$\therefore I_3 = I_1 - I_2$$

$$\therefore I_3 = 3.0 - 7.0 = -4.0$$

negative means direction guessed is wrong, thus is 4Amps to the left.

- The Loop Rule: Based on Law of conservation of Energy

A loop is defined as any closed conducting path in a circuit. If the charges in potential across all circuit elements in the loop are summed, the sum will be zero


$$\sum \Delta V_{\text{loop}} = 0$$

$$\sum V_{\text{rises}} = \sum V_{\text{drops}}$$

What is a Rise or Drop: *conventional current direction*

Resistor		
emf source (battery)		
capacitor		

ex.

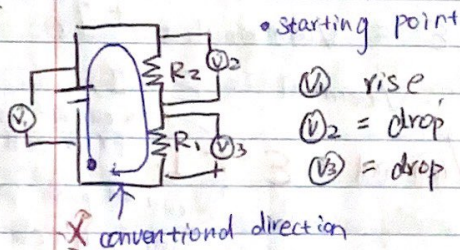


• starting point

- ① rise
- ② = drop
- ③ = drop

$$\sum V_{\text{rise}} = \sum V_{\text{drops}}$$

$$\therefore V_T = V_2 + V_3$$

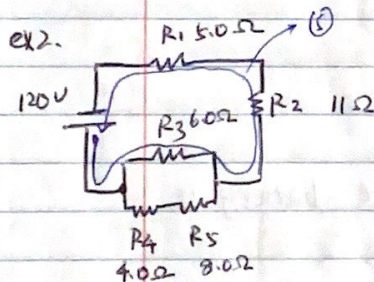

What is V_4 ?

V	I	R
$V_T = 120$	$I_T = 6.0$	$R_T = 20$
① $V_1 = 30$	$I_1 = 6.0$	$R_1 = 5.0$
② $V_2 = 66$	$I_2 = 6.0$	$R_2 = 11$
$V_3 = 24$	$I_3 = 4.0$	$R_3 = 6.0$
③ $V_4 = 8$	$I_4 = 2.0$	$R_4 = 4.0$
④ $V_5 = 16$	$I_5 = 2.0$	$R_5 = 8.0$

$$\textcircled{1} R_T = R_1 + R_2 + \left(\frac{1}{R_3} + \frac{1}{R_4 + R_5} \right)^{-1} = 20 \Omega$$

$$\textcircled{2} V_T = I_T \cdot R_T \therefore I_T = V_T / R_T = 120 / 20 = 6.0 \text{ A}$$

$$\textcircled{3} V_1 = I_1 \cdot R_1 = 6 \times 5 = 30 \text{ V}$$

$$\textcircled{4} V_2 = I_2 \cdot R_2 = 6 \times 11 = 66 \text{ V}$$

$$\textcircled{5} \sum V_{\text{rise}} = \sum V_{\text{drop}}$$

$$V_T = V_3 + V_2 + V_1$$

$$\therefore V_3 = V_T - V_2 - V_1 \therefore V_3 = 120 - 30 - 66$$

$$\therefore V_3 = 24 \text{ V}$$

$$\textcircled{6} V_3 = I_3 \cdot R_3 \therefore I_3 = V_3 / R_3 = 24 / 6 = 4.0$$

$$\textcircled{7} I_4 = I_5 \quad I_{\text{in}} = I_{\text{out}}$$


$$\therefore I_T = I_3 + I_4$$

$$I_4 = 6.0 - 4.0 = 2.0 \text{ A}$$

$$\textcircled{8} V_4 = I_4 \cdot R_4 = 2.0 \times 4.0 = 8$$


$$\textcircled{9} V_5 = I_5 \cdot R_5 = 2.0 \times 8.0 = 16$$

Two Cell Analysis.


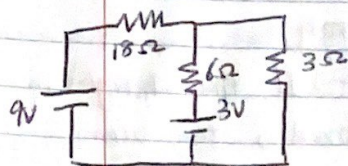


→ Terminal Voltage ←

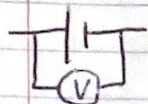- Voltage measured across terminals of chemical cell.




ideal cell
low I circuit

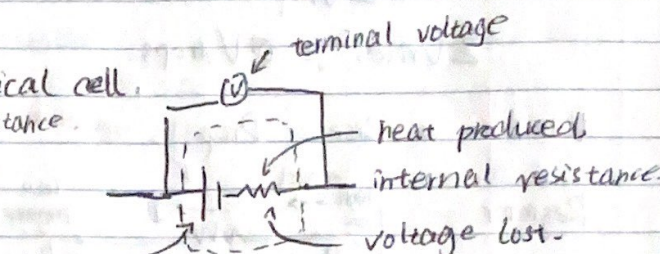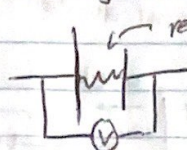

chemical voltage
Real Cell
High I circuit

ex.

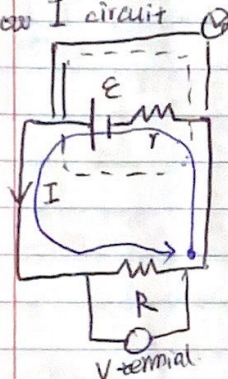

$r = \text{internal resistor}$

$\epsilon = \text{chemical Emf}$

$V_{\text{term}} = \text{Terminal Voltage}$

$$\sum V_{\text{rise}} = \sum V_{\text{drop}}$$

$$\epsilon = V_{\text{terminal}} + Ir$$

$$\therefore V_{\text{terminal}} = \epsilon - Ir$$

$$V_{\text{terminal}} = \epsilon \mp Ir$$

current is drawn from cell (discharge)
current push backwards into cell (charging)

Charging circuit



the current is going to opposite direction, which entails the battery is being charged, thus $V_{\text{terminal}} = \epsilon + Ir$