F= K(R)Q2 Y2 K= 471E0 = 9.0×109
Capacitors Capacitors
- Capacitors are fundamental component used in a variety of electronics applications are used to Stoke energy and charge in form of electric field.
Ability to store charge is defined as Capacitance, C
potential difference across capacitor (V)
Q=CV where C is the capacitance of capacitor. (unit: f/farad)
XC = Q(9/V) = F(forced)
Ex. If a 22 MF capacitor is connected to a 10 V source, the charge is ? Q=CV = Q= $22 \times 10^{-6} \times 10 \text{ V} = 220 \text{ MC}$
Capacitance: Analogy: rubber bands in a bottle: To ensure more charges/bands in bottle, either increase bottle size/capacitance,
or increase the force / Voltage [Q=C*V]
- Construction:
· Composed of 2 conductive plates separator by an insulator.
Charles Canada Wil
Increasing surface area of the plates
Decreasing the spacing between places
$C = KE_0 \frac{A(m^2)}{d(m)}$ unit of $KE_0 (F/m)$ KE_0 is called permittivity
C directly proportions to relative dielectric constant and the plate area.
C is inversely proportional to the distance between the plates,
$\varepsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2/\text{k} \text{ varies with a minimum value of 1}$
Relative Permittivity:
Annumumum Market Company of the Comp

constanting Permittivity: The ratio of the flux density to the electric field intensity in the dielectric: A measure of how easily the dielectric will "permit" the establishment of flux lines within the dielectric Relative & Permittivity: Often called the dielectric constant, it's the natio of the permittivity of any dielectric to that of a vaccum Circuit Symbols for Capacitors Variable capacitor. fixed Capacitor Capacitor works back to original state Capacitors in circuits: Steady States: full/empty - Empty Capacitor. closed switch Full Capacitor: No I flow

Ex. An empty copacitor is in the circuit below when switch is closed, all current will go through the apacitor, lamp will not light up as no I will pass through. steady states When the capacitor is full lafter some time and cannot accept more charge, current will then flow through Lamp instead In reality, the lamp will transition from dim to bright gradually In parallel Capacitors: Think of it as making a capacito " In series Capacitors: Transient Phase: A period of time transition from one steady to the other steady phase Charging Capacitor Graphs: 1=CE 1 1 = E/R current us t Discharging Capacitor Graphs: Q=C8 I=E/R magnitude of arrent.

Capacitors in Circuits = RC circuit T= Q.F (RxC) (unit in seconds/s) In series circuit, the charge on each capacitor stongs the same, the voltage is different depending on its appoitance. In parallel circuits, the voltage across each capacitor is the same, charge depends on its capacitance. Magnetism Q is charge B is magnitism, Most permanent magnets have B makes Moving De in them are called ferromagnetic moving Q creates Magnetism moving Q interacts with Induction . · Each magnet has two poles, North and South. · Mognets always have North pole to Magnetic North: South to magnetic south · There're no magnetic monopoles - one cannot divide a magnet North and South in isolation "Magnetic poles exhibit for interactions: Opposite poles attract and like poles when split, they still to have north and 0 pole. In will remain, S is created 6-6-7shared by magnetic materials is the presence of small regions called A property · Fau elements exhibit magnetic properties in pure state: iron, nickle, gadolinium and dysprosium, there are man-made magnetic materials . The domain model explains how iron an both be a magnet (with an active magnetic field), and magnetic (attracted to a magnet)